

**YAMHANA UNIVERSITY OF SCIENCE & TECHNOLOGY, YMCA FARIDABAD**  
**B.TECH. EXAMINATION (Under CBS)**  
**Elements of Electronics Engineering [E-101]**

3 Hrs.

M. Marks:60

Part -A is compulsory. Attempt any four out of 6 questions from part -B

**Part-A**

- (a) What is slew rate in an OP-AMP? (2)
- (b) Name the different quantity which can be measured by multimeter. (2)
- (c) A crystal has the following parameters:  $L = 0.5H$ ,  $C1 = 0.06pf$ ,  $C2 = 1pf$  and  $R = 5k\Omega$ . Calculate the series and parallel resonant frequencies. (2)
- (d) What is the Barkhausen's criterion of oscillations? (2)
- (e) Write truth table of JK flip flop. (2)
- (f) Differentiate between drift current and diffusion current. (2)
- (g) How a zener diode is different from normal PN junction diode? (2)
- (h) Why some gates are known as universal gates? Name them. (2)
- (i) Name different types of liquid crystal? (2)
- (j) What are characteristics of an ideal opamp? (2)

**PART-B**

- Q.2 (a) Differentiate between combinational & sequential circuits. (3)
- (b) Explain SR flipflop with its diagram & truth table. (3)
- (c) Convert (i)  $(232.92)_{10} = (\dots\dots\dots)_{16}$  (ii)  $(11001100.0101)_2 = (\dots\dots\dots)_{10}$ . (4)
- Q.3 (a) Describe the working of CRO with neat sketches. (5)
- (b) Explain how the resistance of circuit can be measured using multimeter. Explain how does this process is carried out inside multimeter? (5)
- Q.4 (a) Explain construction, working of LED display. Also compare LCD with LED display. (5)
- (b) Explain the applications of OP-AMP as a differentiator and adder. (5)
- Q.5 (a) How is SMPS different from Linear power supply? (5)
- Derive the expression for frequency of oscillation of Wein bridge oscillator. (5)
- Q.6 (a) A transistor has  $I_B = 105 \mu A$  and  $I_C = 2.05 mA$ . Find (i)  $\beta$  of transistor (ii)  $\alpha$  of transistor (iii) emitter current  $I_E$  (iv) Now if  $I_B$  changes by  $27 \mu A$  and  $I_C$  changes by  $+0.65 mA$ , find the new value of  $\beta$ . (5)
- (b) Discuss the working of R-C coupled amplifier with its frequency response and bandwidth. (5)
- Q.7 (a) Discuss breakdown mechanisms in a p-n junction diode. (3)
- (b) An amplifier has a voltage gain of 40 and feedback factor of 0.01. Calculate the Gain with positive & negative feedback. (3)
- (c) Write a short note on: (4)
  - (i) diffusion & storage capacitances
  - (ii) Voltage regulator

SEM

1st