

Time: 3 Hours

Max. Marks:75

- Note: 1. It is compulsory to answer the questions of Part -1. Limit your answers within 20-40 word in this part.
2. Answer any four questions from Part -2 in detail.
3. Different parts of the same question are to be attempted adjacent to each other.
4. Assume suitable standard data wherever required, if not given.

PART -1

- Q1 (a) What is race around condition? (1.5)
- (b) What is the minimum number of flip flops required to design a Mod-12 ripple counter? (1.5)
- (c) Differentiate between ripple and synchronous counter. (1.5)
- (d) What are the various types of shift register? (1.5)
- (e) What are error correcting codes? (1.5)
- (f) What are the various applications of counters? (1.5)
- (g) Differentiate between edge triggering and level triggering. (1.5)
- (h) What is the difference between SRAM and DRAM? (1.5)
- (i) Convert the following: (1.5)
- a) $(2A6)_{16} = (?)_{10}$
- b) $(10011.101)_2 = (?)_{16}$
- c) $(221)_{10} = (?)_8$
- (j) Why do we use ASCII code? (1.5)

PART -2

- Q2 (a) Discuss the working and operation of active pull up type TTL circuit. (8)
- (b) Design and implement a Mod-5 synchronous counter using T-Flip Flop (7)
- Q3 (a) Implement the following expression using a single 8:1 multiplexer. (7)
- $$Y(A,B,C,D) = \sum m(0,1,2,5,7,8,9,14,15)$$
- (b) Design and implement a 2-bit comparator using suitable logic gates. (5)
- (c) What is the resolution in volts of a 10-bit D/A Converter whose full scale output is 5V? (3)
- Q4 (a) What are different types of shift registers? Explain universal shift register in detail. (5)
- (b) Design a binary to Gray Code converter (5)
- (c) Convert S-R Flip Flop to J-K Flip Flop (5)
- Q5 (a) Design a combinational circuit for a common cathode display BCD to 7 segment code converter. (8)
- (b) With a neat circuit diagram explain the operation of a Counter type A/D converter (7)
- Q6 (a) Explain the following terms: (5)
- i) Figure of merit
- ii) Fan out

Examination Roll No.....

- iii) Propagation delay
- iv) Tristate logic
- v) Noise margin

(b) With the help of truth table, Explain the working of J-K Master-slave flip flop. (5)

(c) Discuss the various specifications of a DAC Converter? (5)

Q7 (a) Minimize the expression using K-map and realize using minimum number of gates: (7)
 $F(A,B,C,D) = \Sigma m (0,1,2,3,5,7,8,9,11,14)$

(b) Write a short note on PLA and PAL . Also state the differences. (8)
