

Roll No. ....

Total Pages : 5

**307301**

**December, 2019**

**B.Tech. (EL/EEE)- III SEMESTER  
ELECTRIC CIRCUIT ANALYSIS (ELPC301)**

Time : 3 Hours]

[Max. Marks : 75

**Instructions :**

1. *It is compulsory to answer all the questions (1.5 marks each) of Part-A in short.*
2. *Answer any four questions from Part-B in detail.*
3. *Different sub-parts of a question are to be attempted adjacent to each other.*

**PART - A**

1. (a) What do you mean by an electric network and an electric circuit? (1.5) CO1  
(b) Find the voltage at the terminals of a coil having  $R = 10 \Omega$  and  $L = 15H$  at the instant when the current is 10A and increasing @ 5 A/sec. (1.5) CO2  
(c) What is the phase difference between voltage and current in an RC circuit? (1.5) CO3  
(d) Derive the condition on Z parameters for a reciprocal network. (1.5) CO4  
(e) Explain the concept of source transformation. (1.5) CO1


307301/180/111/243

[P.T.O.  
23/12

- (f) Time constant of RL circuit is given by  $L/R$ . Show that the unit of  $L/R$  is second. (1.5) CO2
- (g) State the advantages of three phase systems. (1.5) CO3
- (h) Express  $Y_{21}$  in terms of ABCD parameters. (1.5) CO4
- (i) State convolution property of Laplace Transform. (1.5) CO2
- (j) Derive the relation between the mutual inductance  $M$  and self-inductance of coils  $L_1$  and  $L_2$ . (1.5) CO3

### PART - B

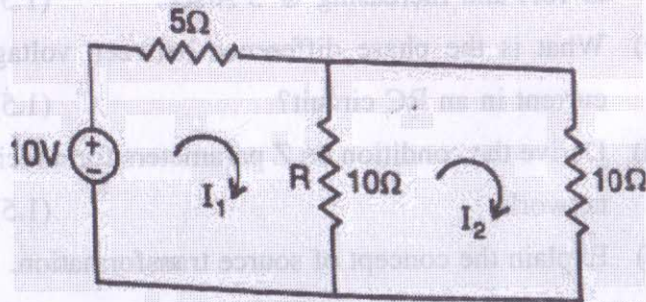
2. (a) Derive the condition for maximum power transfer (7) CO1
- (b) In the circuit shown below the resistance  $R$  is changed from 10 ohms to 5 ohms. Verify the compensation theorem. (8) CO1



307301/180/111/243

2

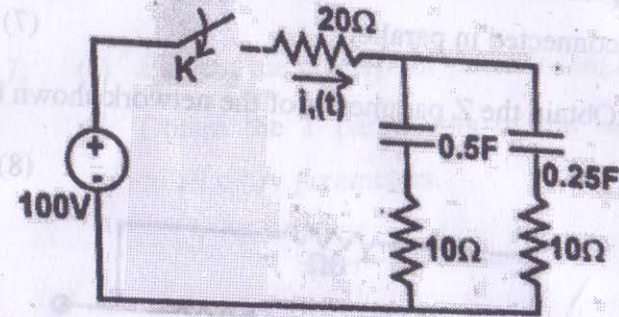
3. (a) In the network shown below the switch is closed at  $t = 0$  and there is no initial charge on either of the capacitances. Find  $i_1(t)$ . (8) CO2



- (b) Prove that for an RLC series circuit the resonant frequency is geometric mean of upper and lower half power frequencies. (7) CO2

4. (a) In the circuit shown below the reactance of the capacitor is  $C_1$  is 4 ohms, the reactance of capacitor  $C_2$  is 8 ohms and the reactance of inductor  $L$  is 8 ohms. A sinusoidal voltage of 120 V is applied to the circuit. Find

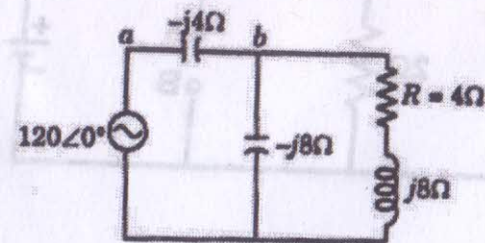- (i) the current in each branch.  
(ii) Power loss in the circuit. (15) CO3




307301/180/111/243

3


[P.T.O.]

5. (a) Prove that overall Y parameters matrix for parallel connected two port network is simply the sum of Y parameters matrices of each individual to port network connected in parallel. (7) CO4

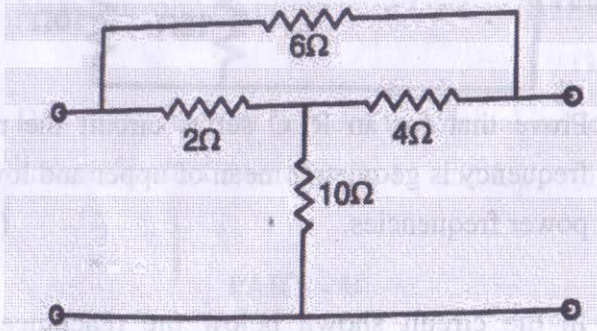- (b) Obtain the Z parameters of the network shown below (8) CO4



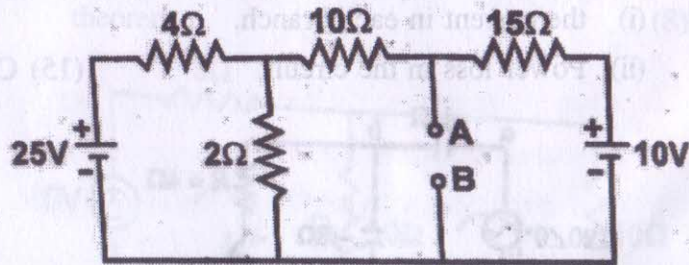6. (a) Obtain the Thevenin equivalent circuit at terminals B of the active network. (8) CO1



- (b) Find the response of a network if  $H(s) = \frac{s^2 + 3s + 5}{(s+1)(s+2)}$  and excitation is  $x(t) = e^{-3t}$ . (7) CO2

7. (a) Explain the concept of power triangle. (5) CO3  
 (b) Obtain the T parameters of the network in terms of all other parameters. (10) CO4

---