

Roll No.

Total

BT/IV/ 2018
POWER ELECTRONICS-I
(EE-206C)

Time : 3 Hours]

[Max. Marks : 75

Instructions :

- (i) Question Paper consists of two parts namely Part-I and Part-II. Part-I consists of 10 small questions of 1.5 marks each and Part-II comprises of 6 questions of 15 marks each.
- (ii) Part-I is compulsory to attempt. Answer any four questions from Part-II.

PART-I

1. (i) What is the significance of di/dt in SCRs?
- (ii) Define reverse recovery time.
- (iii) Define latching current and holding current as applicable to an SCR.
- (iv) Sketch the circuit symbol of (a) IGBT (b) TRIAC (c) UJT (d) MOSFET.
- (v) What is the purpose of dv/dt protection ?
- (vi) What is a snubber network?
- (vii) What is a self-commutation?
- (viii) List five industrial applications of rectifiers.

80744/80/111/256

[P.T.O.

- (ix) What is the cause of circulating current in dual converters?
- (x) Why heat sink is required for connecting the thyristor? (1.5×10=15)

PART-II

2. (a) Describe the different modes of operation of a thyristor with the help of its static V-I characteristics and define terms related to it. (8)
- (b) Draw and explain the working of UJT and RC firing circuits. (7)
3. (a) A 230 V, 1 kW resistive load is connected to a half wave rectifier. Input voltage of the rectifier is 230 V ac. Find the values of (i) output dc power, (ii) output ac power, (iii) input power factor. (9)
- (b) Discuss the operation of Three phase full wave rectifier with appropriate circuit and suitable waveforms. (6)
4. (a) Explain the working of a single phase full wave fully controlled SCR based converter with R L load through the waveforms of supply voltage, load voltage, load current and voltage across the SCR at an firing angle $\alpha = 45$ degree. Assume discontinuous load current. (9)
- (b) Describe the effect of source Inductance on the performance of three phase controlled rectifier with the help of phase voltage waveform. (6)

5. (a) Give the classification of controlled rectifiers ; also give their circuit diagrams along with a brief description of operation. (9)
- (b) Why is the power factor of semiconverters better than that of full converters? (6)
6. (a) Draw two transistor model of thyristor and explain working. (8)
- (b) Describe switching characteristics of power diode. (7)
7. Discuss any *three* of the following :
- (i) Dynamic characteristics of SCR.
- (ii) Commutation Techniques.
- (iii) Series and Parallel operation of Thyristors.
- (iv) Dual Converter. (5×3=15)