

YMCA UNIVERSITY OF SCIENCE & TECHNOLOGY, FARIDABAD

M.Tech Examination (Under CBS)

Sub: AVLSI Design (E-16V 602)

Time: 3Hr

Max Marks 60

Note:-

1. There is two parts in the question paper, namely Part-I and Part -II, Part -I is compulsory and in part -II, there is six questions. Out of six, four question to be attempted.
2. In part-I there are ten questions, each question of 2 Marks and in Part-II each question is 10 Marks.
3. In Case of numerical problems, assume data wherever not provided.

Part-I (2x10 = 20)

Q.No.1 Short answer type (word limit 20-40 words only).

- (a) Define Noise margin and how it is calculated from the graphical characteristics of inverter.
- (b) In which technology Intel i3 and i5 processors are fabricated?
- (c) Define the analog octagon.
- (d) Prove the equivalency between T and pi small signal model for MOSFET.
- (e) Explain the operation of C.S amplifier, when the load is (a) resistive load (b) Diode load (c) current source load.
- (f) For Common gate configuration calculate its input impedance.
- (g) Define Analog IC design flow.
- (h) For Wilson current mirror calculate the output resistance.
- (i) Compare the BJT and MOSFET based source follower configurations.
- (j) Explain how technology scaling impacts gain and bandwidth?

Part-II

Q.1 a) For fig 1. using small signal model analysis calculates the output resistance and gain.

 


Fig. 1

b) What is the need of Darlington configuration and how it works? Derive the relationship for current gain for the Darlington pair.

Q.2 a) Analyze the circuit shown in Fig. 2 to determine the voltage at all nodes and the currents through all branches. Let $V_t = 1V$ and $k'_n \left(\frac{W}{L}\right) = 1mA/V^2$. Neglect the channel-length modulation effect i.e., assume $\lambda = 0$.


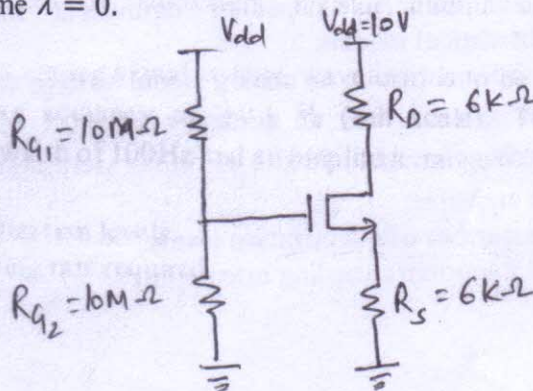


Fig. 2

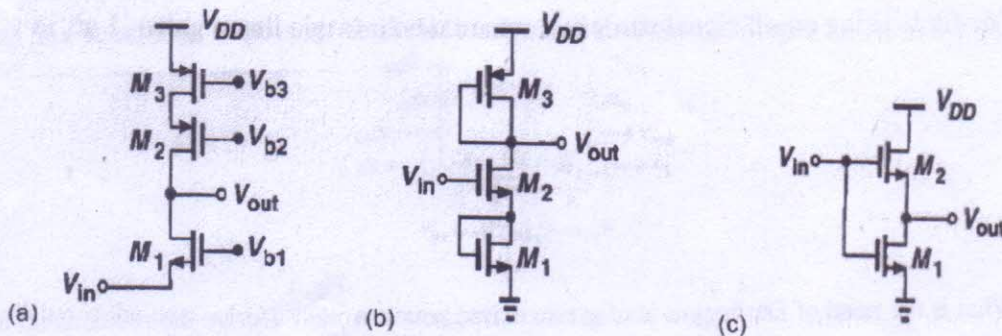- b) What is the need of cascode configuration? Explain in detail with mathematical justification.
- Q.3 a) Calculate the frequency response and gain of uncompensated two stage CMOS op-amp.
- b) Consider a process technology for which $L_{min} = 0.4\mu m$, $t_{ox} = 8nm$, $\mu_n = \frac{450cm^2}{V.s}$, and $V_t = 0.7$.
- Find C_{ox} and k'_n .
 - For a MOSFET with $\frac{W}{L} = 8\mu m/0.8\mu m$, calculate the value of V_{GS} and V_{DSmin} needed to operate the transistor in the saturation region with a dc current $I_D = 100\mu A$.
- For the device in (b), find the value of V_{GS} required to cause the device to operate as a 1000Ω resistor for very small V_{DS} .
- Q.4a) Find the midband gain A_M and the upper 3-db frequency f_H of a CS amplifier fed with a signal source having an internal resistance $R_{sig} = 100k\Omega$. The amplifier has $R_G = 4.7M\Omega$, $R_D = R_L = 15k\Omega$, $g_m = \frac{1mA}{V}$, $r_o = 150k\Omega$, $C_{gs} = 1pF$, and $C_{gd} = 0.4pF$.
- b) Derive the r_{out} for cascode current mirror and plot its output characteristic comparative to basic and Wilson current mirror.
- Q. 5a) For an n-channel MOSFET with $t_{ox} = 10nm$, $L = 1.0\mu m$, $W = 10\mu m$, $L_{ov} = 0.05\mu m$, $C_{sb0} = C_{db0} = 10fF$, $V_0 = 0.6V$, $V_{SB} = 1V$, and $V_{DS} = 2V$, calculate the following capacitance when the transistor is operating in saturation: C_{ox} , C_{ov} , C_{gs} , C_{sb} , C_{db} .
- b) Calculate the small signal voltage gain the given below Fig. 3 (a) to (c).



Q.6 Write a short Note on :

- Explain switched capacitor equivalent resistor circuit with the help of mathematical models.
- The information in an analog signal voltage waveform is to be transmitted over a PCM system with an accuracy of $\pm 0.1\%$ (full scale). The analog voltage waveform has a bandwidth of 100Hz and an amplitude range of -10 to +10 volts.
 - Find the step size.
 - Find the number of quantization levels.
 - Find the minimum sampling rate required.