

Roll No. ....

Total Pages : 6

**322104**

**December, 2019**

**M.Tech. (VLSI) - I SEMESTER**

**Device Modelling for Circuit Simulation (MVLE110)**

Time : 3 Hours]

[Max. Marks : 75

*Instructions :*

1. *It is compulsory to answer all the questions (1.5 marks each) of Part-A in short.*
2. *Answer any four questions from Part-B in detail.*
3. *Different sub-parts of a question are to be attempted adjacent to each other.*
4. *Data sheet is required for 130 nm and 180 nm technology node.*

**PART - A**

1. (a) Write the spice command for ac, dc, transient, noise, temp analysis with full syntax. (1.5)

- (b) Transconductance of MOSFET is greater in linear or in saturation region, justify your statement. (1.5)
- (c) How many types of SPICE MOS models are available in literature, write the full name of at least five models? (1.5)
- (d) How many types of power dissipation are possible in CMOS integrated circuits, write the mathematical formulation for each? (1.5)
- (e) Explain series and parallel operation of pass transistor logic circuit. (1.5)
- (f) Write the mathematical model for sub-threshold current equation in a MOSFET. (1.5)
- (g) Define the MOSFET capacitance Model in different region of operation. (1.5)
- (h) Define logical effort and how it helps in improving the performance of integrated circuits. (1.5)
- (i) How channel length modulation is measured? (1.5)
- (j) What is the need for modelling a system? (1.5)

## PART - B

2. The circuit of Fig. 1 shows different implementations of an inverter whose output is connected to a capacitor, do all calculation in  $0.13 \mu\text{m}$ . (15)

 


Fig. 1

- (a) Which one of the circuits consumes static power when the input is high?
- (b) Which one of the above circuits consumes static power when the input is low?
- (c)  $V_{OH}$  of which circuit(s) is 1.2 V? (d)  $V_{OL}$  of which circuit(s) is 0 V?
- (d) The proper functionality of which circuit(s) depends on the size of the device?

3. Calculate  $V_{OH}$  and  $V_{OL}$  of the circuits in Fig. 1 (15)

4. (a) Derive the formulation for transconductance with and without body bias for MOSFET. And address the merits of both the case with mathematical justification. (8)

(b) An 8 input AND gate is to be designed to drive a load of 200 fF but is limited to an input capacitance of 20 fF. Since a single 8 input CMOS NAND gate is out of the question, choose two configurations that are more suitable and identify the solution with the fastest speed. (7)

5. In each of the circuit of Fig. 2, determine the self capacitance at the output assuming step changes at the input shown. (15)

 


Fig. 2

6. (a) Derive the value of logic effort for gates with equal delays for inverter, NAND and NOR and calculate the same for multi input case for one, two and three input signal to logic gates. (8)
- (b) Calculate the delay for an inverter chain and do inverter sizing for optimal delay (Optimization-FO4 Delay). (7)
7. How to choose a flexible substrate for Printed Electronics? And what types of flexible substrates are possible. Explain the mechanism for printing a simplest device like LED. (15)
-

## USEFUL PHYSICAL AND MATERIAL CONSTANTS

| Name                                      | Symbol          | Value                  | Units                      |
|---|-----------------|------------------------|----------------------------|
| Electron Charge                           | $q$             | $1.6 \times 10^{-19}$  | C                          |
| Boltzmann's Constant                      | $k$             | $1.38 \times 10^{-23}$ | J/°K                       |
| Room Temperature                          | $T$             | 300                    | °K (27°C)                  |
| Thermal Voltage                           | $V_{th}=kT/q$   | 26                     | mV (at 27°C)               |
| Dielectric Constant of Vacuum             | $\epsilon_0$    | $8.85 \times 10^{-14}$ | F/cm                       |
| Dielectric Constant of Silicon            | $\epsilon_{si}$ | $11.7\epsilon_0$       | F/cm                       |
| Dielectric Constant of SiO <sub>2</sub>   | $\epsilon_{ox}$ | $3.97\epsilon_0$       | F/cm                       |
| Intrinsic Carrier Concentration           | $n_i$           | $1.45 \times 10^{10}$  | /cm <sup>3</sup> (at 27°C) |
| Carrier Saturation Velocity<br>In Silicon | $v_{sat}$       | $8 \times 10^6$        | cm/s                       |
| Aluminum Resistivity                      | $\rho_{Al}$     | 2.7                    | $\mu\Omega$ -cm            |
| Copper Resistivity                        | $\rho_{Cu}$     | 1.7                    | $\mu\Omega$ -cm            |
| Tungsten Resistivity                      | $\rho_W$        | 5.5                    | $\mu\Omega$ -cm            |

## ENGINEERING SCALE FACTORS

|       |       |            |
|-------|-------|------------|
| G     | giga  | $10^9$     |
| M     | mega  | $10^6$     |
| k     | kilo  | $10^3$     |
| c     | centi | $10^{-2}$  |
| m     | milli | $10^{-3}$  |
| $\mu$ | micro | $10^{-6}$  |
| n     | nano  | $10^{-9}$  |
| p     | pico  | $10^{-12}$ |
| f     | femto | $10^{-15}$ |
| a     | atto  | $10^{-18}$ |

## METER CONVERSION FACTORS

$$1 \mu\text{m} = 10^{-4} \text{cm} = 10^{-6} \text{m}$$

$$1 \text{m} = 10^2 \text{cm} = 10^6 \mu\text{m}$$

$$0.1 \mu\text{m} = 100 \text{nm}$$

$$1 \text{\AA} = 10^{-8} \text{cm} = 10^{-10} \text{m}$$

For 322104(MVLE 110)

**USEFUL DESIGN PARAMETERS (simplified)**

| Name  | Symbol           | 0.18 $\mu$ m        |                      | 0.13 $\mu$ m        |                      | Units                    |
|---|------------------|---------------------|----------------------|---------------------|----------------------|--------------------------|
|   |                  | NMOS                | PMOS                 | NMOS                | PMOS                 |                          |
| Channel Length<br>(rounded for convenience) | L                | 200nm               | 200nm                | 100nm               | 100nm                | nm                       |
| Supply Voltage                              | V <sub>DD</sub>  | 1.8                 | 1.8                  | 1.2                 | 1.2                  | V                        |
| Oxide Thickness                             | t <sub>ox</sub>  | 35                  | 35                   | 22                  | 22                   | Å                        |
| Oxide Capacitance                           | C <sub>ox</sub>  | 1.0                 | 1.0                  | 1.6                 | 1.6                  | $\mu$ F/cm <sup>2</sup>  |
| Threshold Voltage                           | V <sub>TO</sub>  | 0.5                 | -0.5                 | 0.4                 | -0.4                 | V                        |
| Body-effect term                            | $\gamma$         | 0.3                 | 0.3                  | 0.2                 | 0.2                  | V <sup>1/2</sup>         |
| Fermi Potential                             | 2  $\phi_F$      | 0.84                | 0.84                 | 0.88                | 0.88                 | V                        |
| Junction Capacitance<br>Coefficient         | C <sub>jo</sub>  | 1.6                 | 1.6                  | 1.6                 | 1.6                  | fF/ $\mu$ m <sup>2</sup> |
| Built-in Junction<br>Potential              | $\phi_B$         | 0.9                 | 0.9                  | 1.0                 | 1.0                  | V                        |
| Grading Coefficient                         | m                | 0.5                 | 0.5                  | 0.5                 | 0.5                  | -                        |
| Nominal Mobility<br>(low vertical field)    | $\mu_o$          | 540                 | 180                  | 540                 | 180                  | cm <sup>2</sup> /V-s     |
| Effective Mobility<br>(high vertical field) | $\mu_e$          | 270                 | 70                   | 270                 | 70                   | cm <sup>2</sup> /V-s     |
| Critical Field                              | E <sub>c</sub>   | 6 × 10 <sup>4</sup> | 24 × 10 <sup>4</sup> | 6 × 10 <sup>4</sup> | 24 × 10 <sup>4</sup> | V/cm                     |
| Critical Field x L                          | E <sub>c</sub> L | 1.2                 | 4.8                  | 0.6                 | 2.4                  | V                        |
| Effective Resistance                        | R <sub>eff</sub> | 12.5                | 30                   | 12.5                | 30                   | k $\Omega$ /ف            |

| Name                         | Symbol           | Value    | Units         |
|------------------------------|------------------|----------|---------------|
| Gate Capacitance Coefficient | C <sub>g</sub>   | 2        | fF/ $\mu$ m   |
| Self Capacitance Coefficient | C <sub>eff</sub> | 1        | fF/ $\mu$ m   |
| Wire Capacitance Coefficient | C <sub>w</sub>   | 0.1-0.25 | fF/ $\mu$ m   |
| Al Wire Resistance           | R <sub>Al</sub>  | 25-60    | m $\Omega$ /ف |
| Cu Wire Resistance           | R <sub>Cu</sub>  | 20-40    | m $\Omega$ /ف |
| Wire Inductance              | L <sub>eff</sub> | 40-50    | pH/ $\mu$ m   |