

YMCA UNIVERSITY OF SCIENCE AND TECHNOLOGY, FARIDABAD

B.Tech 1st Semester Examination

Electrical Technology

Paper E-105

Time:- Three Hours

Maximum Marks:-60

Note:- (i) Question no.1 is compulsory from Part-I.


(ii) Attempt any four questions from Part-II.

PART-I – (2x10 = 20 Marks)


- Q.1.a) Explain the terms amplitude, cycle, time period and phase difference. (2)
- b) Define the terms: active power, reactive power, apparent power. (2)
- c) The equation of an alternating current is $i = 42.42 \sin 628t$. Determine; its maximum value; frequency; RMS value; average value and form factor. (2)
- d) What is the significance of j-operator? (2)
- e) State Norton's theorem. (2)
- f) What are the similarities between magnetic circuit and electrical circuit? (2)
- g) What are the causes of low power factor? (2)
- h) What are eddy currents? (2)
- i) What is the function of commutator in a dc machine? (2)
- j) Compare star-connection and delta-connection with reference to a three phase system. (2)

PART-II – (4x10 = 40 Marks)

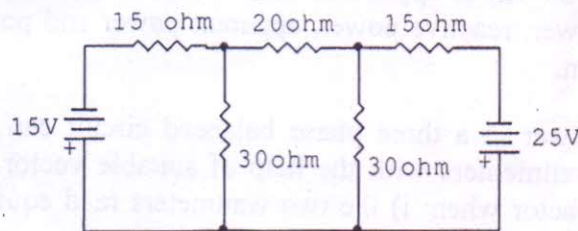
- Q.2.a) Determine currents in each branch in a given network using mesh analysis. (5)



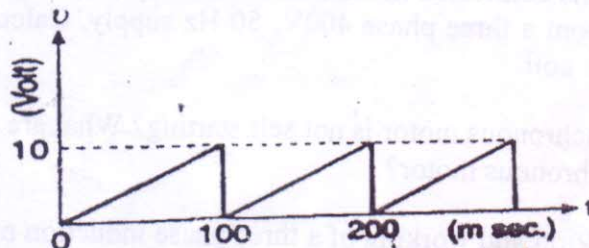- b) For a given waveform, determine: frequency of waveform; wave equation for $0 < t < 100$ m sec; rms value; average value and form factor. (5)



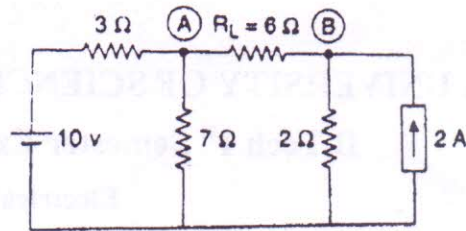- Q.3.a) In the given circuit, find the power delivered to the 6 ohm resistor by using Thevenin's theorem. (5)



- b) A sinusoidal a.c. voltage applied to a single phase circuit at $t=0$ has rms values of 200V, frequency 50 Hz, and instantaneous value of $200\sqrt{2}$ V. The current is 5A and has a 0.5 lag p.f. Write (i) expression for instantaneous value of voltage, and current; (ii) value of circuit parameter in ohm, and impedance in complex number form, and (iii) value of instantaneous voltage and current at $t=0.0125$ s. (5)
- Q.4.a) A steel ring has mean diameter of 20 cm, a cross-section area of 25 cm^2 and a radial air-gap 0.8 mm cut across it. When excited by a current of 1A through a coil of 1000 turns wound on the ring core, it produced an air gap flux of 1mWb. Neglecting leakage and fringing calculate: the relative permeability of steel and the total reluctance of the magnetic circuit. (5)
- b) What is resonance? What are the properties of the circuit when it is in resonance? Derive the condition for resonance in a series RLC circuit and draw a phasor diagram. (5)
- Q.5.a) Explain as to what you understand by (i) static, (ii) dynamic inducement of electromotive force. Illustrate by the help of simple sketches. (5)
- b) A coil having resistance of 5 ohm and an inductance of 0.02 H is arranged in parallel with another coil having resistance of 1 ohm and inductance of 0.08 H. When a supply of 100V, 50 Hz is applied to the circuit, determine: branch current, total current, active power, reactive power, apparent power and power factor. Also draw the phasor diagram. (5)
- Q.6.a) Prove that the power in a three phase balanced circuit can be deduced from the reading of two wattmeters with the help of suitable vector diagram. Discuss the nature of power factor when: i) the two wattmeters read equal and opposite values and, (ii) the one wattmeter reads zero. (5)
- b) Three similar coils connected in star, takes a total power of 1.5kW at a power factor of 0.2 lagging from a three phase 400V, 50 Hz supply. Calculate the resistance and inductance of the coil. (5)
- Q.7.a) Explain why synchronous motor is not self starting? What are the starting methods of three phase synchronous motor? (5)
- b) Explain construction and working of a three phase induction motor. (5)