

Roll No.

Total Pages : 4

307401

May, 2019

B.Tech. IV SEMESTER

Digital Electronics (ELPC-401)

Time : 3 Hours

Max. Marks : 75

Instructions :

1. *It is compulsory to answer all the questions (1.5 marks each) of Part-A in short.*
2. *Answer any four questions from Part-B in detail.*
3. *Different sub-parts of a question are to be attempted adjacent to each other.*

PART-A

1. (a) What is the function of clock in sequential circuits? (1.5)
- (b) What is race around condition? (1.5)
- (c) Differentiate between ripple and synchronous counter. (1.5)
- (d) Which logic family has highest speed of operation? (1.5)
- (e) What is the significance of ASCII code? (1.5)

307401/220/111/158

[P.T.O.
16/5

- (f) What are the various types of Read only memories? (1.5)
- (g) Differentiate between edge triggering and level triggering. (1.5)
- (h) What is the resolution in volts of a 10-bit D/A Converter whose full scale output is 5V ? (1.5)
- (i) Perform (20-42) using 2's complement method. (1.5)
- (j) What are various types of error correcting codes? (1.5)

PART-B

- 2. (a) Design and implement a Mod-5 up/down counter using JK-Flip Flop. (7)
- (b) Simplify the logic function using Quine-McCluskey method.
 $F(A, B, C, D) = \sum m(1, 2, 3, 8, 9)$ (5)
- (c) Convert the following :
 $(2A6)_{16} = (?)_{10}$
 $(10011.101)_2 = (?)_{16}$
 $(221)_{10} = (?)_8$. (3)
- 3. (a) Write short notes on PLA and PAL. (8)
- (b) Simplify the logic expression using K-map
 $F(A, B, C, D) = \sum m(0, 1, 5, 7, 10, 14) + d(2, 4)$. (4)
- (c) Implement $Y(A, B, C) = \sum m(0, 4, 5, 7)$ using 3 : 8 line decoder. (3)

- 4. (a) Discuss in detail the different types of shift registers. (5)
- (b) Convert S-R to T Flip Flop. (5)
- (c) Implement $(A + C)(A + D)(A + B + C)$ using NOR gates only. (5)
- 5. (a) Design a combinational circuit for a common anode display BCD to 7 segment code converter. (8)
- (b) With a neat circuit diagram explain the operation of a Successive Approximation type A/D converter. (7)

- 6. (a) Explain the following terms:
 (i) Fan in.
 (ii) Fan out.
 (iii) Propagation delay.
 (iv) Tristate logic.
 (v) Hold time. (5)
- (b) With the help of truth table, explain the working of J-K Master-slave flip flop. (5)
- (c) Simplify the following expression :
 (i) $Z = A[B + C(AB + AC)]$
 (ii) $Z = \overline{A} \overline{B} C + \overline{(A + B + C)} + \overline{A} \overline{B} C D$. (5)

7. (a) Explain the working of a basic TTL NAND gate with a neat diagram. Explain the following output configurations :

(i) Open collector output.

(ii) Totem pole output. (8)

(b) Implement following Boolean function using 8 : 1 multiplexer.

$$F(A, B, C, D) = \sum m(0, 1, 3, 4, 5, 8, 9, 15) \quad (7)$$
