

Roll No. ....

Total Pages : 3

**007304****Mar. 2022****B.Tech. (EL) - III SEMESTER****Electric Circuit Analysis (ELPC-301)**

Time : 90 Minutes]

[Max. Marks : 25

*Instructions :*

1. *It is compulsory to answer all the questions (1 mark each) of Part-A in short.*
2. *Answer any three questions from Part-B in detail.*
3. *Different sub-parts of a question are to be attempted adjacent to each other.*


**PART-A**

1. (a) Explain compensation Theorem. (1)  
(b) Mention the limitations of Ohm's Law. (1)  
(c) Define time constant of RL circuit. (1)  
(d) A  $15 \Omega$  resistor, an inductor with  $8 \Omega$  inductive reactance, and a capacitor with  $12 \Omega$  capacitive reactance are in parallel across an ac voltage source. Calculate the circuit impedance. (1)  
(e) State dot rule for coupled coils. (1)  
(f) A coil having inductance of 4 H and resistance of 2 ohms are connected across a 20 V dc source, find the steady state flowing current. (1)

- (g) Define coefficient of coupling. (1)
- (h) What is the Laplace transform of delayed impulse function. (1)
- (i) Write hybrid parameters equation. (1)
- (j) Differentiate between zero input response and zero state response. (1)


**PART-B**

2. For the given network

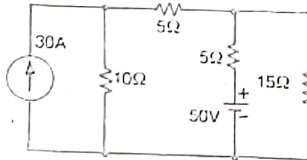

- (a) Draw the equivalent Norton's circuit. (3)
- (b) Determine the current through 15 ohm resistor. (2)

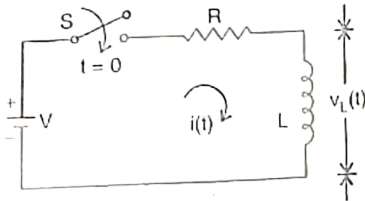3. (a) Consider a series RL circuit as shown. The switch S is closed at time  $t = 0$ . Find the current  $i(t)$  through and voltage across the resistor. (5)



- 4. Derive the condition for series interconnection of two-2-port networks. (5)
- 5. Find the Laplace transform of  $t \cos wt u(t)$ . (5)
- 6. (a) Find the circuit element if the applied voltage and currents are  $v(t) = 50 \sin (2000t + 65^\circ)$  and  $i(t) = 8 \sin (2000t + 95^\circ)$ . Find Z and draw the impedance diagram and phasor diagram. (3)
- (b) Write the characteristics features of an ideal transformer. (2)