

Roll No.

Total Pages : 3

311104

January 2023

BCA 1st SEMESTER

Logical Organization of Computer-I (BCA-17-104)

Time : 3 Hours]

[Max. Marks : 75

Instructions :

1. *It is compulsory to answer all the questions (1.5 marks each) of Part-A in short.*
2. *Answer any four questions from Part-B in detail.*
3. *Different sub-parts of a question are to be attempted adjacent to each other.*
4. *Use of Scientific calculator is not allowed.*

PART-A

1. (a) Define the following terms: Bit, Nibble, Byte. (1.5)
- (b) Explain De Morgan's Law. (1.5)
- (c) Find the Binary equivalent of $(22A.3)_{16}$. (1-5)
- (d) Perform 47-36 using 2's complement method. (1.5)
- (e) Encode the decimal number 37 to gray code. (1.5)
- (f) Difference between Minterm and Maxterm. (1.5)
- (g) Explain XOR Gate. (1.5)
- (h) Why we add Don't care conditions in our Boolean Expression? (1.5)

311104/500/111/420

426 [P.T.O.]

- (i) Design parallel binary adder. (1.5)
 (j) What is AND-OR-INVERT Gate? (1.5)

PART-B

2. (a) Explain Floating point representation of number. Represent $(625.125)_{10}$ using single-precision floating point representation. (10)
 (b) Write note on BCD codes. (5)
3. (a) Simplify and Minimize using K-map the following Function (7)
 $F(A, B, C, D) = \Sigma m(0, 2, 5, 7, 8, 10, 13, 15)$.
 (b) Find out the values of X, Y & Z in following : (8)
 $(523.225)_{10} = (X)_2 = (Y)_8 = (Z)_{16}$.
4. Design a circuit with the help of K-map which convert 4-bit binary number into Excess-3 code and also write the expression for each binary bit. (15)
5. (a) Simplify the following expression using Boolean Algebra : (5)
 (i) $XY + XYZ + X(Y + XY)$.
 (ii) $C(B + C)(A + B + C)$.
 (iii) $(AB'(C + BD) + A'B')C$.
 (b) Explain Decoder and also design the circuit for 3 to 8 Decoder. (10)

6. (a) Design and explain the parallel Binary Adder/Subtractor circuit. (10)
 (b) Difference between Decoder and Encoder. (5)
7. (a) What is Multiplexer? Design the circuit for 4*1 Multiplexer. (8)
 (b) Design a 1-bit magnitude comparator with three outputs: $A > B$, $A < B$ and $A = B$. (7)