

May 2023, Reappear

## B.Sc. (H) PHYSICS SEMESTER -IV

## Basic Instrumentation Skills (SECP-03)

Time: 3 Hours

Max. Marks:75

- Instructions:**
1. It is compulsory to answer all the questions (1.5 marks each) of Part -A in short.
  2. Answer any four questions from Part -B in detail.
  3. Different sub-parts of a question are to be attempted adjacent to each other.

PART -A

- Q1 (a) Distinguish between precision and accuracy of an instrument? (1.5)
- (b) Can a multimeter be used for measuring very low resistances? What are the (1.5) limitations in such measurements?
- (c) List the advantages of digital instruments over analog instruments. (1.5)
- (d) What are the advantages of an electronic voltmeter over conventional (1.5) voltmeter?
- (e) What is the difference between regulated and unregulated power supply? (1.5)
- (f) Calculate the value of multiple resistance on the 50 V range of a dc voltmeter (1.5) that uses a 500  $\mu$ A meter movement with an internal resistance of 1 k $\Omega$
- (g) What is the role of Visual persistence in CRO? (1.5)
- (h) What are the different types of AC millivoltmeter? (1.5)
- (i) Draw the block diagram of a digital multimeter (1.5)
- (j) Discuss the frequency ratios of two signals on the basis of the Lissajous (1.5) patterns formed.

PART -B

- Q2 (a) Explain the principles of measurement of dc voltage, dc current, ac voltage, ac (10) current and resistance by using a multimeter.
- (b) Discuss the loading effect of a multimeter with the help of an example. (5)
- Q3 (a) Draw the block diagram of electronic voltmeter and explain its working (10) principle.
- (b) Explain the working principle of digital voltmeter. (5)
- Q4 (a) Explain how the frequency, voltage, and phase difference is measured using a (10) CRO.
- (b) What are the Lissajous figures? Discuss how they are produced in a dual (5) channel CRO.
- Q5 (a) Explain the working principle of DSO. (10)
- (b) A Maxwell Bridge is used to measure inductive impedance. At balance, the (5) bridge constants are  $C_1 = 0.01 \mu\text{F}$ ,  $R_1 = 470 \text{ k}\Omega$ ,  $R_2 = 5.1 \text{ k}\Omega$ ,  $R_3 = 100 \text{ k}\Omega$ . Find the series equivalent of unknown impedance.

- Q6 (a) Draw the Circuit of Anderson's Bridge and derive the balancing conditions. (10)  
(b) A De-Sauty's bridge is operating at 1 kHz frequency. The constants for the bridge are  $R_1 = 4 \text{ k}\Omega$ ,  $R_2 = 2 \text{ k}\Omega$  and  $C_1 = 3 \text{ }\mu\text{F}$ . Find the value of the other capacitor  $C_2$ . (5)
- Q7 (a) Draw the Block diagram of a CRO. Give the specifications of CRO. Explain the functioning of its horizontal deflection system. (10)  
(b) Briefly discuss the role of 'Time Base circuit' and 'synchronization circuit' in CRO. (5)

\*\*\*\*\*