

7. (a) Discuss the various specifications of a DAC Converter?
With a neat circuit diagram explain the working of a
Weighted resistor type Digital to Analog Converter.

CO3 (10)

- (b) Write a short note on semiconductor memories.

CO4 (5)

Roll No.

Total Pages : 4

007403

May 2023

**B.Tech. (EL) IV SEMESTER
DIGITAL ELECTRONICS (ELPC401)**

Time : 3 Hours]

[Max. Marks : 75

Instructions :

1. *It is compulsory to answer all the questions (1.5 marks each) of Part-A in short.*
2. *Answer any four questions from Part-B in detail.*
3. *Different sub-parts of a question are to be attempted adjacent to each other.*

PART-A

1. (a) What is the difference between a synchronous and a asynchronous counter? CO2 (1.5)
- (b) Differentiate between PLA and PAL. CO4 (1.5)
- (c) What are the various types of clocks in sequential circuits? CO2 (1.5)
- (d) What is the resolution in volts of a 10-bit D/A Converter whose fullscale output is 5V? CO3 (1.5)
- (e) Which of the digital logic families is the fastest among all? CO1 (1.5)

- (f) Display the decimal numbers (97 and 19) in Excess-3 code. CO1 (1.5)
- (g) What do you understand by the problem of current hogging? CO1 (1.5)
- (h) What is the significance of ASCII code? CO1 (1.5)
- (i) Perform (20-42) using 1's complement method. CO1 (1.5)
- (j) What is a race around condition? CO2 (1.5)

PART-B

2. (a) Perform the following conversions: CO1 (5)
- (i) $(49056)_{10} = (?)_{16}$
- (ii) $(10101)_2 = (?)_{10}$
- (iii) $(2AB)_{16} = (?)_8$
- (iv) $(C20)_{16} = (?)_2$
- (v) $(287)_{10} = (?)_8$
- (b) Encode data bits 0011 into the 7-bit even parity Hamming code. CO1 (5)
- (c) Discuss the working of a parallel-in serial-out (PISO) register in detail. CO2 (5)
3. (a) Reduce the expression $F(A, B, C, D) = \sum m(0, 1, 2, 3, 5, 7, 8, 9, 10, 12, 13)$ using K-map and implement using NAND gates only. CO2 (7.5)

- (b) With a neat circuit diagram explain the operation of a Counter type A/D converter. CO2 (7.5)

4. (a) Explain the following terms : CO1 (5)
- (i) Fan in.
- (ii) Figure of merit.
- (iii) Propagation delay.
- (iv) Tristate logic.
- (v) Passive pull up.
- (b) Implement following Boolean function using a 8 : 1 multiplexer.
 $F(A, B, C, D) = \sum m(0, 1, 3, 4, 5, 8, 9, 15)$. CO2 (5)
- (c) Design a combinational circuit for a common anode display BCD to 7 segment code converter. (for any one segment) CO2 (5)
5. (a) Design a 4-bit BCD to gray code converter using logic gates. CO2 (7.5)
- (b) Carry out the conversion of S-R Flip-Flop to J-K Flip-Flop CO2 (7.5)
6. (a) Explain the working of TTL logic family with active pull up configuration with suitable diagrams and truth table. CO1 (7.5)
- (b) Design and implement a Mod-5 up/down counter using JK-Flip-Flop. CO2 (7.5)