

December 2023

**B. Tech (CE/CSE/ECE/ME) Re-Appear 1st Sem.
Basic Electrical Engineering (ESC-101)**

Time: 3 Hours

Max. Marks:75

- Instructions:**
1. It is compulsory to answer all the questions (1.5 marks each) of Part -A in short.
 2. Answer any four questions from Part -B in detail.
 3. Different sub-parts of a question are to be attempted adjacent to each other.

PART -A

- Q1 (a) Distinguish between loop and mesh? (1.5)
- (b) State and explain Kirchoff's current and voltage laws? (1.5)
- (c) What do you understand by self induced e.m.f and mutually induced e.m.f? (1.5)
- (d) Explain how a sinusoidal e.m.f is generated? (1.5)
- (e) Explain with mathematical expression that power consumed in a pure capacitance is zero? (1.5)
- (f) Describe the basic features of a balanced 3- phase system? (1.5)
- (g) Name the various parts of a D.C machine and give the function of each part? (1.5)
- (h) Draw the torque-slip curve of a 3-phase induction motor and mark on it the starting torque, maximum torque and full load torque? (1.5)
- (i) Discuss the requirements of a good inverter? (1.5)
- (j) What are line-commutated inverters? (1.5)

PART -B

- Q2 (a) State the maximum power transfer theorem. Show that for maximum power transfer $RL = R_{th}$ and explain its importance? (7)
- (b) State and explain Superposition theorem how is it applied for solving a network? (8)
- Illustrate the application of the theorem with reference to an appropriate electric network?
- Q3 (a) For a half wave rectified alternating current, find (1) Average value (2). RMS value (10)
- (3). Form factor (4) Peak Factor
- (b) Describe the condition of Series resonance using appropriate circuit diagram and waveforms. (5)

Q4 (a) Explain the principle of working of an auto- transformer. In what ways does an auto-transformer differ from a conventional two-winding transformer? What are its application and disadvantages? (7.5)

b) A parallel circuit consists of a $2.5 \mu\text{F}$ capacitor and a coil whose resistance and inductance are 15Ω and 260 milli-Henry respectively. Determine (1) the resonant frequency (2) Quality factor of the coil (3) Dynamic impedance of the circuit? (7.5)

Q5 (a) A single phase transformer with a ratio 5:1 has primary resistance of 0.4 ohm and reactance of 1.2 ohm and the secondary resistance of 0.01 ohm and reactance of 0.04 ohm. Determine the percentage regulation when delivering 125 A at 600 V at (1). 0.8 power factor lagging (2). 0.8 power factor leading? (7.5)

(b) Explain the construction and working principle of a miniature circuit breaker (MCB) (7.5)

Q6 (a) Clearly explain difference between squirrel cage and slip-ring induction motors? (7.5)

(b) Explain the advantages of making field system rotating and armature stationary in case of an synchronous alternator? (7.5)

Q7 (a) Describe the working of a single-phase half- bridge inverter. What is its main drawback? Explain how this drawback is overcome? (8)

(b) What is the objective of Earthing? Explain different methods of earthing? (7)
