

Roll No. ....

Total Pages : 3

007301

December 2023

**B.Tech (EL) III Semester**  
**ELECTRICAL CIRCUIT ANALYSIS**  
**(ELPC-301)**

Time: 3 Hours]

[Max. Marks. : 75

Instructions :

1. It is compulsory to answer all the questions (1.5 marks each) of Part-A in short.
2. Answer any four questions from Part-B in detail.
3. Different sub-parts of a question are to be attempted adjacent to each other.
4. Assume relevant data wherever required.

**PART-A**

1. (a) What is the condition on transmission parameters for a reciprocal network. (1.5)  
(b) Explain the concept of duality and dual networks. (1.5)  
(c) Draw the phasor diagram of RL and RC circuit. (1.5)  
(d) Explain the term-Power triangle. (1.5)  
(e) Explain the significance of zero input response and zero state response. (1.5)


007301/150/111/409

[P.T.O.]

- (f) What are the advantages of three phase system?(1.5)
- (g) Compare voltage resonance and current resonance.(1.5)
- (h) Obtain the Z parameters of the network in term of Y Parameters. (1.5)
- (i) Explain the reason for negative sign in  $I_2$  current of ABCD Parameter's equation. (1.5)
- (j) Draw the equivalent circuit of a 2-port network in terms of Z parameters. (1.5)


### PART-B

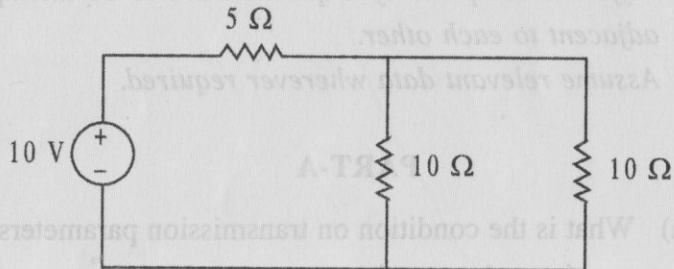2. (a) In the circuit given below, the resistance R is changed from 10 ohms to 5 ohms. Verify compensation theorem. (10)



- (b) State and Explain Reciprocity Theorem using suitable example. (5)
3. (a) Explain the significance of time constant of RL Circuit. (5)

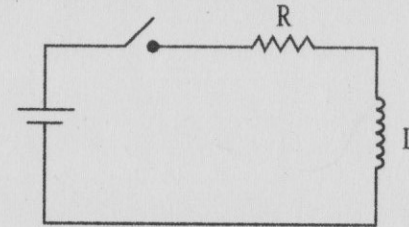- (b) Consider a series R-L circuit as shown. The switch S is closed at  $t = 0$ . Find the current  $i(t)$  through and voltage across the resistor and inductor. (10)



4. Derive the condition for series and parallel interconnection of two port networks. (15)
5. (a) For the current  $i(t) = 5U(t) - 3e^{-2t}$ . find  $I(s)$  and hence determine the value of  $i(0+)$  and  $i(\infty)$ . (8)
- (b) Derive the expression for Q factor of a coil. (7)
6. (a) If  $f_1(t) = 2u(t)$  and  $f_2(t) = e^{-3t}u(t)$ . Determine the convolution between  $f_1$  and  $f_2$ . (8)
- (b) Explain Dot convention in coupled circuit. (7)
7. (a) A voltage of  $230V \angle 45^\circ$ , 50 Hz is applied across an RLC series circuit where the input current is  $10 \angle -30^\circ$  A. If  $R = 5$  ohms,  $X_L = j8$  ohms. Find the value of capacitance reactance. (10)
- (b) Write short note on ideal transformer. (5)