

401 / 1
9/12
20
d/c

Sr. No 321309

December 2023

B.Sc. (Physics) B.Sc. - III SEMESTER

Electrical Circuits & Network Skills (SECP-02)

Time: 3 Hours

Max. Marks: 75

- Instructions:
1. It is compulsory to answer all the questions (1.5 marks each) of Part -A in short.
 2. Answer any four questions from Part -B in detail.
 3. Different sub-parts of a question are to be attempted adjacent to each other.

PART -A

- Q1 (a) State Ohm's law in reference to dc circuits. (1.5)
- (b) How much heat is produced by 2 kW electric heater when it is operated for 30 minutes? (1.5)
- (c) Distinguish between AC and DC electricity. (1.5)
- (d) A coil of resistance 1000Ω and inductive reactance 200Ω is connected across supply voltage of 230 V. Find the supply current. (1.5)
- (e) What is the phase relationship between the supply voltage and current flowing through a purely inductive circuit? (1.5)
- (f) What is meant by a fuse? On what principle does it operate? (1.5)
- (g) What is meant by conductivity and how is it related with resistivity? (1.5)
- (h) Write e.m.f equation of a dc motor. (1.5)
- (i) What is meant by power factor? How can it be improved? (1.5)
- (j) What is the difference between a wire and a cable? (1.5)

PART -B

- Q2 (a) Obtain the expression of rise and decay of current through a R-L circuit. (10)
- (b) Define resistance. How does increase in temperature affect the resistance of (i) conductors and (ii) insulators? (5)
- Q3 (a) Explain how alternating quantities may be represented by complex numbers? (7)
- (b) Add the following vectors given in rectangular form and illustrate graphically too. (8)
- $A = 16 + j 12, B = -6 + j 10.4$
- Q4 What is a transformer? Describe its construction, principle and working with the help of neat diagrams. Also, describe the losses involved. (15)
- Q5 (a) Differentiate between voltmeter and ammeter. (7)
- (b) What are three phase series circuits? Explain its two types of star and delta connections. (8)
- 321309/20/11/1

- Q6 (a) Give a detailed explanation of principles of measurement of voltage, current and resistance with a multimeter. (10)
- (b) The total capacitance of two capacitors is $0.03\mu\text{F}$ when joined in series and $0.16\mu\text{F}$ when connected in parallel. Find the capacitance of each capacitor. (5)
- Q7 Write short notes on the following: (15)
- (a) Relays
 - (b) Kirchoff's laws
 - (c) Preparation of extension board
