

335403

May 2019

B.Sc. (Physics)-4th Semester

DIGITAL SYSTEMS AND APPLICATIONS

(BPH 403)

Time : 3 Hours]

[Max. Marks : 75

Instructions :

- (i) *It is compulsory to answer all the questions (1.5 marks each) of Part-A in short.*
- (ii) *Answer any four questions from Part-B in detail.*
- (iii) *Different sub-parts of a question are to be attempted adjacent to each other.*

PART-A

1. (a) Write the decimal equivalent of the binary number 1010010. (1.5)
- (b) Find the difference between 43 and 32 using 2's compliment. (1.5)
- (c) If an OR gate has four inputs and one input is high and other three are low. What is the output? (1.5)

- (d) How to obtain symmetrical waveform in Astable multivibrator? (1.5)
- (e) What is the basic storage element in digital circuits? (1.5)
- (f) Why is a hexadecimal number system called as an alpha numeric number system? (1.5)
- (g) Prove that $(A + B)(\bar{A} + B) \bar{B} = 0$. (1.5)
- (h) What is the importance of SiO_2 during the IC fabrication? (1.5)
- (i) How many AND, OR and EXOR gates are required for the configuration of full adder? (1.5)
- (j) What is clock frequency of 8085 microprocessor? (1.5)

PART-B

2. (a) Design a circuit that counts the number of 1's present in 3 inputs A, B and C. Its output is a two-bit number $X_1 X_0$, representing that count in binary. Assume active-HIGH logic. (i) Write the truth table for this circuit. (ii) Find the minimized logic equations for outputs X_1 and X_0 using a K-map. (10)
- (b) Design a 3-bit binary synchronous down-counter using J-K flip-flops. (5)

3. (a) Implement the function $F = (AB + A'B')(CD' + C'D)$ using (i) NAND gates (ii) NOR gates. (5)
- (b) Simplify the following Boolean function using 4-variable map
 $F(w, x, y, z) = \Sigma(2, 3, 10, 11, 12, 13, 14, 15)$. (5)
- (c) Show how to make a 2-input NAND out of 2-input NOR gates. (5)
4. (a) Write the advantage of EPROM over PROM. (5)
- (b) Astable multivibrator operating at 150 Hz has a discharge time of 2.5 ms. Find the duty cycle of the circuit. (5)
- (c) Determine the time period of a monostable 555 multivibrator. (5)
5. (a) Differentiate between Combinational & Sequential Circuits. (5)
- (b) Design a 4 bit shift register in parallel in serial out mode. (10)
6. (a) What are the advantages of ion implantation technique in comparison to diffusion? (5)
- (b) What are the basic processes involved in fabricating ICs using planar technology? Briefly explain every step. (10)

7. (a) What are the different Flags in 8085 microprocessor? (5)
- (b) Draw the block diagram of 8085 microprocessor and explain the working of every component. (10)
-