

Roll No.

Total Pages : 3

204104

Dec., 2018

BCA, Ist Semester

LOGICAL ORGANIZATION OF COMPUTER-1

(BCA-17-104)

Time : 3 Hours]

[Max. Marks : 75

Instructions :

(i) *It is compulsory to answer all the questions (1.5 marks each) of Part -A in short.*

Answer any four questions from Part -B in detail.

Different sub-parts of a question are to be attempted adjacent to each other.

PART-A

1. (a) Find the number of locations in memory if 16-bit address bus is used? (1.5)
- (b) Find the octal equivalent of $(111100101)_2$: (1.5)
- (c) Define : bit, byte, word. (1.5)
- (d) What is the size of memory if FFFF is the last address that can be referenced for memory chip? (1.5)
- (e) State De-Morgan's law with an example. (1.5)

- (f) Represent -222 in signed 2's complement notation. (1.5)
- (g) Convert BCD 268 into binary, octal and hexadecimal representation. (1.5)
- (h) Convert from infix to postfix notation :

$$A+B*[C*D+E*(F+G)]$$
 (1.5)
- (i) How can the parity bit be used to check a given code word in odd parity system? (1.5)
- (j) Why is floating point number more difficult to represent and process than a fixed point integer? (1.5)

PART-B

2. (a) Using signed 2's complement representation, perform the arithmetic operations given below with binary numbers and with negative numbers. Use 7 bits to accommodate each number together with its sign. In each case determine if there is an overflow.
- (i) $(+35) + (+40)$
- (ii) $(-35) + (-40)$ (10)
- (b) Write note on different Character codes. Explain with suitable examples. (5)
3. (a) Simplify and minimize using K-Map the following function
- $$F = \sum (0,2,3,5,7,9,11,13,14)$$
- (8)
- (b) Find the POS form for the boolean function
- $$F(A,B,C,D) = \sum (0,1,2,5,8,9,10)$$
- (7)

4. (a) Simplify the Boolean expression using Boolean algebra
- (i) $\bar{x}\bar{y}z + \bar{x}yz + x\bar{y}$
- (ii) $xyz + \bar{x}z + yz$ (6)
- (b) Implement the following functions using NAND and inverter gates
- $$F = AB + A'B' + B'C$$
- (5)
- (c) What is parity checker? Using logic gates, Construct a 4-bit even parity generator. (4)
5. (a) Design a 5×32 decoder using 3×8 decoder. Explain with proper tabulation. (8)
- (b) Implement the function using
- $$\text{MUX } F = \Sigma(0,1,3,4,8,9,15)$$
- (7)
6. (a) List the truth table for 3-variable XOR function
- $$Z = A \oplus B \oplus C$$
- (6)
- (b) A lighting system used at the staircase makes use of two switches with one being at the top and other at the bottom of the stairs. Make a truth table for this given system. Give its logical equation in SOP form. Also, Realize the circuit using minimum (i) NAND (ii) NOR gates. (9)
7. (a) Design a 4-bit magnitude comparator with three outputs : $A > B$, $A < B$ and $A = B$. (7)
- (b) Implement a BCD to seven segment converter. (8)