

Roll No.

Total Pages : 4

425104

December, 2019

M.Tech. (Power Systems)-I SEMESTER

Pulse Width Modulation for PE Converters (MPS 110A)

Time : 3 Hours]

[Max. Marks : 75

Instructions :

1. *It is compulsory to answer all the questions (1.5 marks each) of Part-A in short.*
2. *Answer any four questions from Part-B in detail.*
3. *Different sub-parts of a question are to be attempted adjacent to each other.*
4. *Assume any missing data.*

PART - A

1. (a) What is pulse width modulation control of converters? (1.5)
- (b) What is modulation index? (1.5)
- (c) What is sinusoidal PWM? (1.5)
- (d) How is the output voltage of a sinusoidal PWM control converter varied? (1.5)

425104/30/111/452

[P.T.O.
17/12

- (e) What is a four quadrant converter? (1.5)
- (f) What is the effect of chopping frequency on the load ripple current? (1.5)
- (g) What is the purpose of overmodulation? (1.5)
- (h) What is third-harmonic PWM? (1.5)
- (i) What are the reasons for adding a filter on the inverter output? (1.5)
- (j) What are the types of multilevel inverters? (1.5)

PART - B

- 2. (a) Explain the principle of pulse width modulation with the help of waveforms. (8)
- (b) Comment on the harmonics in three-phase PWM inverters. (7)

- 3. (a) The three-phase, six step inverter has a star connected load with $R = 8\Omega$ and $L = 2 \text{ mH}$. The inverter frequency is 50 Hz and the dc input voltage E is 200 V. (i) Derive the expression for $i(t)$ as a Fourier series. (ii) Determine the RMS phase voltage at fundamental frequency and RMS line current. (10)
- (b) What are the advantages and disadvantages of PWM Inverters? (5)

4. (a) Compare and contrast the features of square wave and sine wave PWMs. (7)
- (b) Explain the technique of reduction of low order harmonics using PWM. (8)
5. (a) Explain how the voltage control of a three phase VSI is achieved (i) by controlling the dc link voltage (ii) by using multiple inverters, and (iii) by using pulse width modulation. (10)
- (b) How is constant torque operation achieved with a PWM inverter? (5)
6. (a) How many SPDT switches are needed for a three and four level inverter? Explain. (6)
- (b) The holding current of thyristors in the single phase full converter is $I_H = 500$ mA and the delay time is $t_d = 1.5$ μ s. The converter is supplied from a 120 V, 60 Hz supply and has a load of $L = 10$ mH and $R = 10$. The converter is operated with a delay angle of $\alpha = 30^\circ$. Determine the minimum value of gate pulse width t_G . (9)

7. Discuss any *two* of the following :
- (i) Zero space vector placement modulation strategies.
 - (ii) PWM for multilevel inverters.
 - (iii) PWM for voltage unbalance.

(15)