

Roll No.

Total Pages : 3

312301

December, 2019

B.Tech. (Fashion & Apparel Engg. / Civil Engg.)

III SEMESTER

Basic Electronics (ESC201)

Time : 3 Hours]

[Max. Marks : 75

Instructions :

1. *It is compulsory to answer all the questions (1.5 marks each) of Part-A in short.*
2. *Answer any four questions from Part-B in detail.*
3. *Different sub-parts of a question are to be attempted adjacent to each other.*

PART - A

1. (a) What is an ideal diode? Draw the voltage-current characteristics of ideal diode. (1.5)
- (b) What is the need of output filters for rectifiers? Discuss. (1.5)
- (c) What is IC regulator? Explain the 7805 voltage regulator. (1.5)
- (d) What is Wein bridge oscillator? Discuss. (1.5)

312301/890/111/51

**[P.T.O.
11/12**

- (e) Give the difference between analog and digital signals. (1.5)
- (f) What are universal gate? Design all basic gates with universals gates. (1.5)
- (g) Design full adder using half adders. (1.5)
- (h) What is a Flip-Flop? Design D flips-flop using SR flip-flop. (1.5)
- (i) What is the difference between microprocessor and microcontroller? Discuss. (1.5)
- (j) What is Barkhausen's criteria for oscillation? Discuss. (1.5)

PART - B

- 2. (a) What is a zener diode? How it works as voltage regulator? Explain. (7.5)
- (b) Draw the circuit diagram of Full wave bridge rectifier and derive the expression to find out the ripple factor and efficiency. (7.5)
- 3. (a) Draw the input and output characteristic for NPN transistor in Common emitter configuration. (7.5)
- (b) Draw the frequency response of CE configuration and discuss why gain falls at lower and higher frequency regions. (7.5)

- 4. (a) What is an ideal Operational amplifier? Explain the characteristics of an ideal Op-Amp. (7.5)
- (b) Explain the operation of Op-Amp based integrator? What is practical integrator? (7.5)
- 5. (a) Discuss the operation of 555 timer as mono stable multi vibrator with circuit diagram. (7.5)
- (b) Derive the relation to find closed loop gain in case on inverting feedback operational amplifier. (7.5)
- 6. (a) Draw the circuit diagram of RC phase shift oscillator and explain the operation. (7.5)
- (b) Simplify the Expression

$$Y = \sum_m (7, 9, 10, 11, 12, 13, 14, 15)$$
 using the K-maps. (7.5)
- 7. (a) What is the need of modulation? Compare AM and FM techniques. (7.5)
- (b) What is shift register? Discuss its types and applications. (7.5)