

752104**Mar. 2022****M.Sc. (Phy) I SEMESTER****Electronic Devices and Integrated Circuits (MPH-104)**

Time : 90 Minutes]

[Max. Marks : 25

 **Instructions :**

1. *It is compulsory to answer all the questions (1 mark each) of Part-A in short.*
2. *Answer any three questions from Part-B in detail.*
3. *Different sub-parts of a question are to be attempted adjacent to each other.*

PART-A

1. (a) Write two advantages and limitations of ICs. (1)
- (b) What are the linear and digital ICs? (1)
- (c) In common base connection $I_c = 0.96$ milliamperes and base current is 0.05 milliamperes. What is the value of alpha? (1)
- (d) Compare JFET and BJT four points. (1)
- (e) Define break down and saturation region. (1)
- (f) Define power supply rejection ratio and input offset current. (1)
- (g) Convert $(2047)_{10}$ to hexadecimal number. (1)

- (h) Calculate the address lines required for an 8K byte memory chip. (1)
- (i) A ripple counters are also called (1)
- (j) Calculate the number of select line required in 1-to-4 demultiplexer. (1)

PART-B

2. (a) How you fabricate an NPN transistor? (3)
- (b) Explain photolithographic process. (2)
3. (a) Explain how OP-AMP is used as difference amplifier. (2)
- (b) Explain the functional block diagram of IC-555 timer. (3)
4. Write short notes on multiplexer and demultiplexer. (5)
5. (a) Draw the equivalent circuit of a MOSFET operating in enhancement mode. (3)
- (b) Explain characteristic curves of JEFT. (2)
6. (a) Draw and explain working of Master-slave JK flip-flop. (2)
- (b) What is shift register? What are the different configuration of shift registers? (3)